

TO: Bally Arcade computer users.

An add-on circuit which improves the <u>audio</u> and <u>video</u> signals, optimizing for recording and/or transmission.

This add-on circuit gives the computer user a line level audio signal output and a composite video signal output. It is a lowest-possible-cost solution to a https://doi.org/10.1001/journal.org/

This add-on circuit was designed and prototyped by Dan Sandin; copied and documented by Phil Morton. For assistance contact Phil at (312) 666-5628, Chicago, Illinois.

For Bally Arcade computer users who are not connected into the ongoing Sandin IMAGE PROCESSOR cybernet, you probably should simply collect the parts (see PARTS LIST) and wire-wrap this circuit.

The following circuit diagram and 2X printed circuit board pictorial can be directly copied by Sandin IMAGE PROCESSOR builders using parts already on hand. The circuit is a slight variation on the "standard driver" used so frequently through-out the IP. We used 1/4 of a #217 board to build the circuit on.

You can do a "neat" job by using either chassis-mount connectors, mounting them in the top plastic "fin", or cable-mount connectors by enlarging the RF Cable hole to run the audio and video cables out. We got away with using RG 174/U (coax) for both audio and video.

If you remove the RF Modulator from your computer then the BNC video out will deliver black-and-white composite video only; no color. This may be desirable for special applications which assume colorizing "down stream" in time.

Remove the five phillips-head screws on the bottom of the computer; the top plaster will now come off. Pull the RF Modulator off the 8 pin connector; solder to pins #1(video), #2(+10 volts), #3(audio). Pin #1 is closest to the heat sink and the front of computer.

Pin #8 = -5 volts

Pin #7 = B-Y

Pin #6 = R-Y

Pin #5 = +2.5 volts

Pin #4 = Chroma


Pin #3 = Audio

Pin #2 = +10 volts

Pin #1 = Video

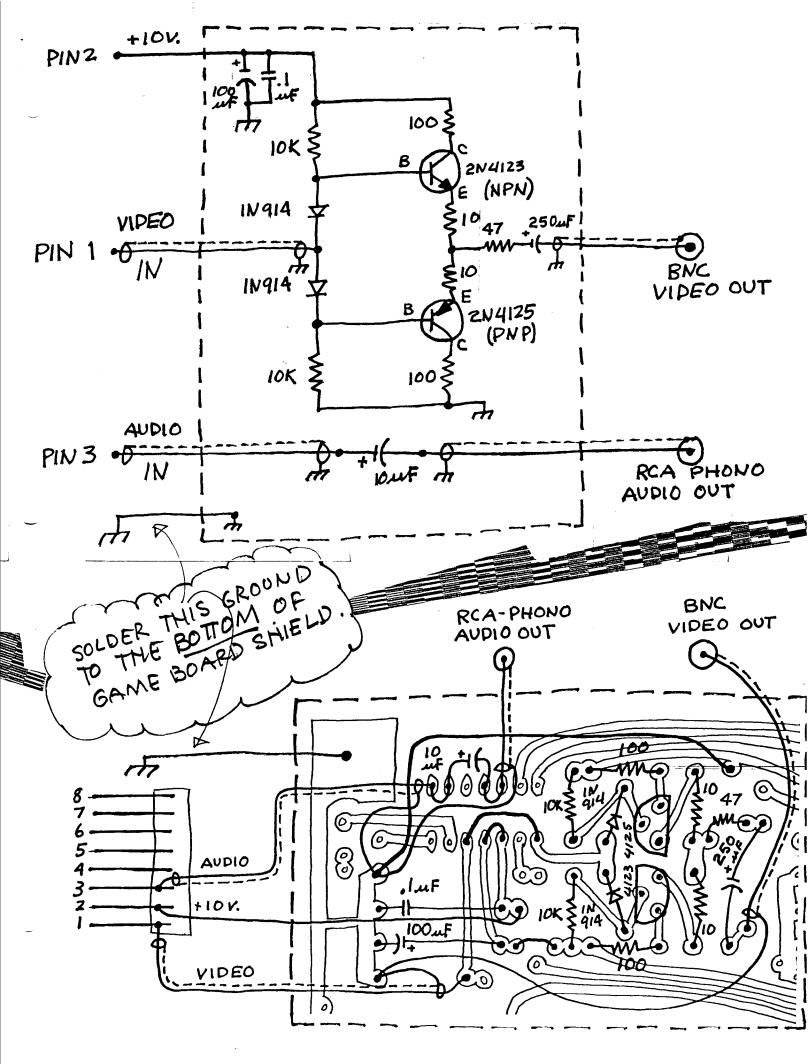"...enjoy your clean pictures and sounds!" - PM





PARTS LIST

Resistors:

- 47Ω 1/4 watt
- 10Ω 1/4 watt 2
- 2 100Ω 1/4 watt
- $10k\Omega$ 1/4 watt

Capacitors:

- .luF 50wvdc cer. disc.
- 10uF 25wvdc electrolytic
- 100uF 25wvdc electrolytic 250uF 12wvdc electrolytic 1

Transistors:

2N4125 (PNP)

2N4123 (NPN) 1

Diodes:

2 1N914

Wire/cable:

4 feet RG 174/U (coax)

2 feet hook-up, grounding, jumping wire

Connectors:

RCA phono-female (chassis \underline{or} cable mount) BNC video-female (chassis \underline{or} cable mount)

PC Board:

1/4 of a #217 board (standard driver in IP)

